

Week 13 Worksheet Solutions

More Electrodynamics

Jacob Erlichman

April 13, 2026

Exercise 1. A capacitor C is charged up to a voltage V and connected to an inductor L in series at time $t = 0$.

- Griffiths 7.27.* Find the current in the circuit as a function of time.
- Show that the total energy of the configuration is constant at any time t , and find this constant.
- Since the induced emf is

$$\mathcal{E} = -L \frac{dI}{dt}$$

and

$$C = \frac{Q}{V},$$

we have that

$$\frac{d^2 I}{dt^2} = -\frac{I}{LC}.$$

It follows that a general solution for $I(t)$ is given by

$$I(t) = A \sin(\omega t) + B \cos(\omega t),$$

where $\omega = 1/\sqrt{LC}$. Since $I(0) = 0$, we should set $B = 0$. Now, at $t = 0$, we have

$$\begin{aligned} V_0 &= -L \left. \frac{dI}{dt} \right|_{t=0} \\ &= -LA\omega. \end{aligned}$$

Hence,

$$A = -\frac{V_0}{L\omega}.$$

The solution for I is then

$$I(t) = -V_0 \sqrt{\frac{C}{L}} \sin\left(\frac{t}{\sqrt{LC}}\right).$$

b) The energy stored in the inductor is $\frac{1}{2}LI^2$. Similarly, the energy stored in the capacitor is $\frac{1}{2}CV^2$. We already know I , so we need to figure out V . We can do this using $CV = Q$, which implies

$$C \frac{dV}{dt} = I.$$

Hence,

$$V(t) = V_0 \cos\left(\frac{t}{\sqrt{LC}}\right),$$

where we note that the integration constant is 0 since $V(0) = V_0$. Now, we can compute

$$\frac{1}{2}LI^2 + \frac{1}{2}CV^2 = \frac{1}{2}CV_0^2.$$